

## 9.3 System Wire Sizing Exercise

**Problem:** Using the sample PV system below, calculate the **current (amps)** in the various portions of the system by answering each of the questions. This system consists of the following specifications and equipment:

- DC system voltage = 24 volts.
- Ten 100-watt modules, each with nominal module voltage of 12 volts. The short circuit current ( $I_{sc}$ ) of each is 7.2 amps and the maximum power current ( $I_{mp}$ ) of each is 6.2 amps.
- Eight batteries, each is 6 volts and rated at 350 amp-hours.
- One charge controller that is 24 volts and rated for 60 amps.
- One 2500-watt inverter with an input DC voltage of 24 volts and an output AC voltage of 120 volts.
- Total connected DC load is 500 watts at 24 volts.

### 1. First draw the system

Determine the **amps** in various circuits on the DC side of a PV system that powers both DC and AC loads.

2. Between panels and controller
3. Between controller and batteries
4. Between batteries and DC load
5. Between batteries and inverter