

S-parameters


MUSE

Material developed by Prof. L. Dunleavy, USF

2-Port Parameters

- Recall Z-Parameters:

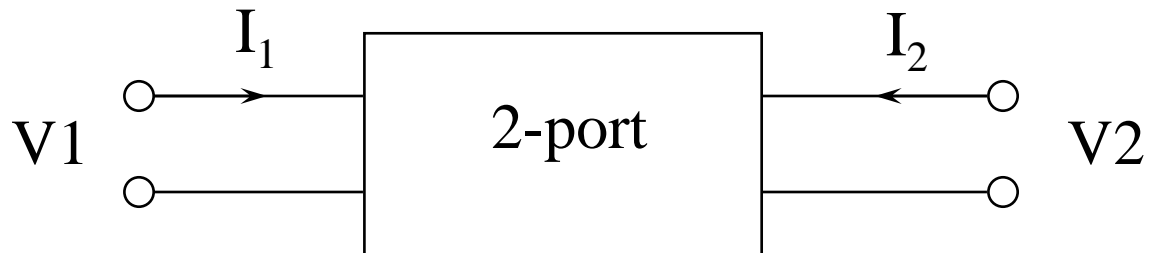
$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \end{aligned} \implies \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{Z}_{11} & \mathbf{Z}_{12} \\ \mathbf{Z}_{21} & \mathbf{Z}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$



2-Port Parameters

- Recall Z-Parameters:
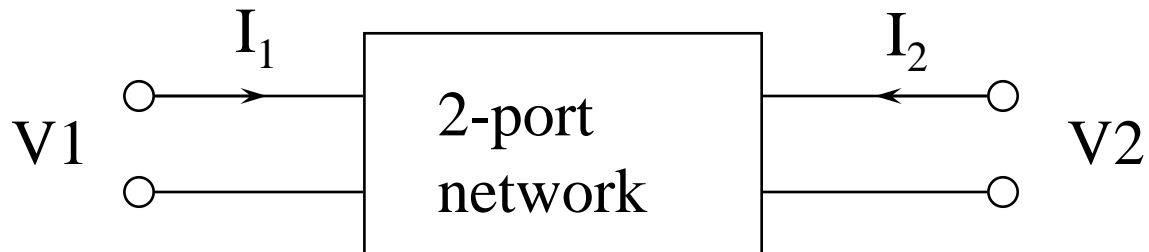
$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \end{aligned} \implies \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{Z}_{11} & \mathbf{Z}_{12} \\ \mathbf{Z}_{21} & \mathbf{Z}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix}$$



2-PORT Parameters (cont'd)

- Y-Parameters:

$$\begin{aligned} I_1 &= Y_{11}V_1 + Y_{12}V_2 \\ I_2 &= Y_{21}V_1 + Y_{22}V_2 \end{aligned} \quad \Rightarrow \quad \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

- h-Parameters:

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned} \quad \Rightarrow \quad \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

2-Port Parameters (cont'd)

- 2-port Parameter Determination:

$$\left. \begin{aligned} h_{11} &= \frac{V_1}{I_1} \Big|_{V_2=0} \\ h_{21} &= \frac{I_2}{I_1} \Big|_{V_2=0} \end{aligned} \right\} \text{(Put a Short Circuit at Port \#2)}$$

$$\left. \begin{aligned} h_{12} &= \frac{V_1}{V_2} \Big|_{I_1=0} \\ h_{22} &= \frac{I_2}{V_2} \Big|_{I_1=0} \end{aligned} \right\} \text{(Put an Open Circuit at Port \# 1)}$$

S-Parameters

At high RF and Microwave frequencies direct measurement of Y-, Z-, or H- parameters is difficult due to:

- Unavailability of equipment to measure RF/MW total current and voltage.
- Difficulty of obtaining perfect opens/shorts
- Active devices may be unstable under open/short conditions.


S-Parameters

- For a two-port device there are four S-parameters S_{11} , S_{21} , S_{12} , and S_{22}
- S_{11} , and S_{22} are simply the forward and reverse reflection coefficients, with the opposite port terminated in Z_0 (usually 50 ohms.)
- S_{21} and S_{12} are simply the forward and reverse gains assuming a Z_0 source and load (again usually 50 ohms).

S-Parameters (cont'd)


- S-Parameters:

$$\begin{aligned} \mathbf{b}_1 &= \mathbf{S}_{11}\mathbf{a}_1 + \mathbf{S}_{12}\mathbf{a}_2 \\ \mathbf{b}_2 &= \mathbf{S}_{21}\mathbf{a}_1 + \mathbf{S}_{22}\mathbf{a}_2 \end{aligned} \implies \begin{bmatrix} \mathbf{b}_1 \\ \mathbf{b}_2 \end{bmatrix} = \begin{bmatrix} \mathbf{S}_{11} & \mathbf{S}_{12} \\ \mathbf{S}_{21} & \mathbf{S}_{22} \end{bmatrix} \begin{bmatrix} \mathbf{a}_1 \\ \mathbf{a}_2 \end{bmatrix}$$

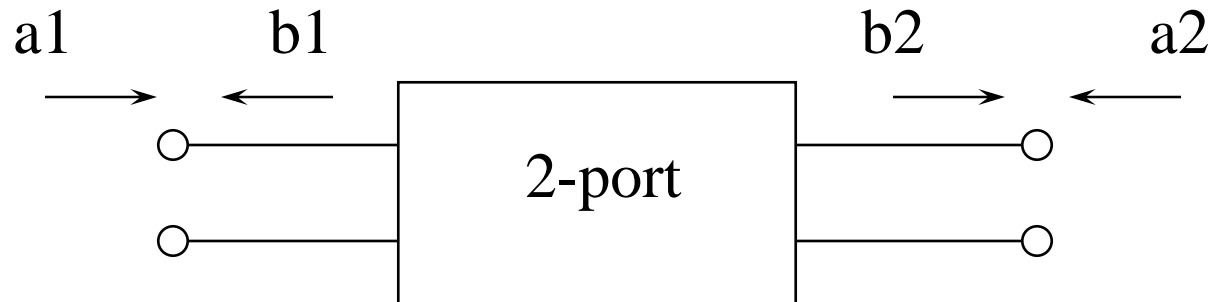

S-Parameters (cont'd)

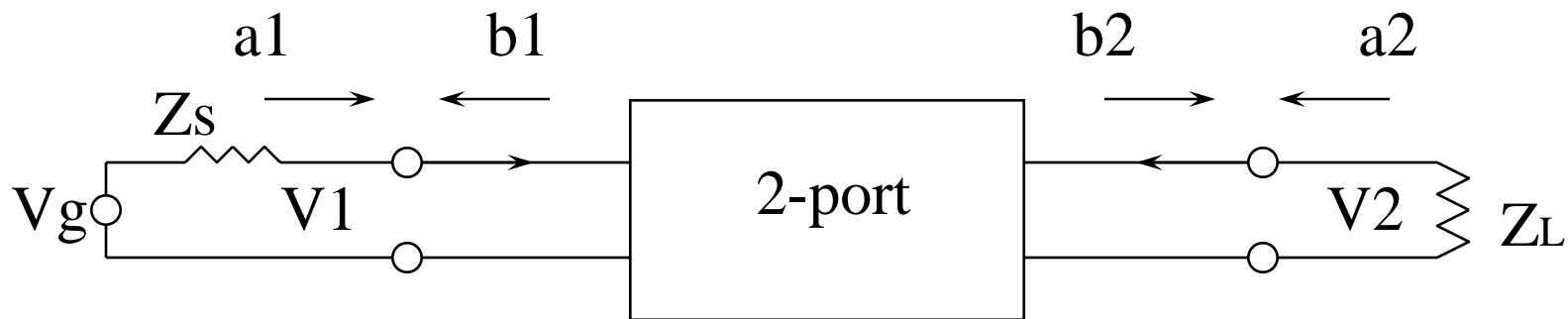- Q. So what's the deal with the a's and b's?



- A. a_1 and a_2 are incident waves; b_1 and b_2 are reflected waves

Incident & Reflected Waves: Simplified Case: $Z_1=Z_s=Z_2=Z_L=Z_0$ (real)

$$a_1 = \frac{V_1 + Z_0 I_1}{2\sqrt{Z_0}} = \frac{\text{Incident port 1 voltage}}{\sqrt{Z_0}} = \frac{E_{i1}}{\sqrt{Z_0}}$$

$$a_2 = \frac{V_2 + Z_0 I_2}{2\sqrt{Z_0}} = \frac{\text{Incident port 2 voltage}}{\sqrt{Z_0}} = \frac{E_{i2}}{\sqrt{Z_0}}$$

$$b_1 = \frac{V_1 - Z_0 I_1}{2\sqrt{Z_0}} = \frac{\text{reflected port 1 voltage}}{\sqrt{Z_0}} = \frac{E_{r1}}{\sqrt{Z_0}}$$

$$b_2 = \frac{V_2 - Z_0 I_2}{2\sqrt{Z_0}} = \frac{\text{reflected port 2 voltage}}{\sqrt{Z_0}} = \frac{E_{r2}}{\sqrt{Z_0}}$$

S-Parameter Determination

$$s_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0} = 0 \quad = \underline{\text{Input reflection coefficient } \Gamma_{in}}$$

for case of $Z_L=Z_0$

$$s_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0} = 0 \quad = \underline{\text{Forward transmission (insertion) gain}}$$

for case of $Z_L=Z_0$


$$s_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0} = 0 \quad = \underline{\text{Reverse transmission (insertion) gain}}$$

for case of $Z_s=Z_0$


$$s_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0} = 0 \quad = \underline{\text{Output reflection coefficient } \Gamma_{out}}$$

for case of $Z_s=Z_0$


Desired Measurement Conditions

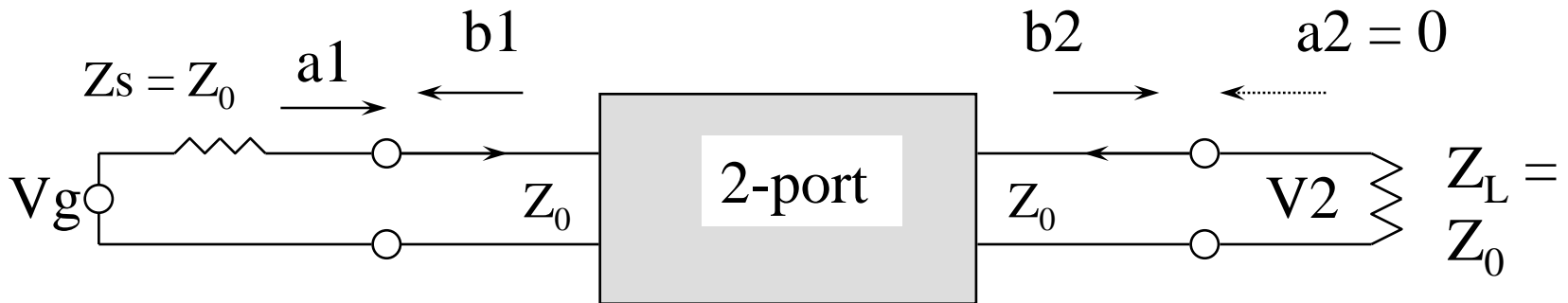

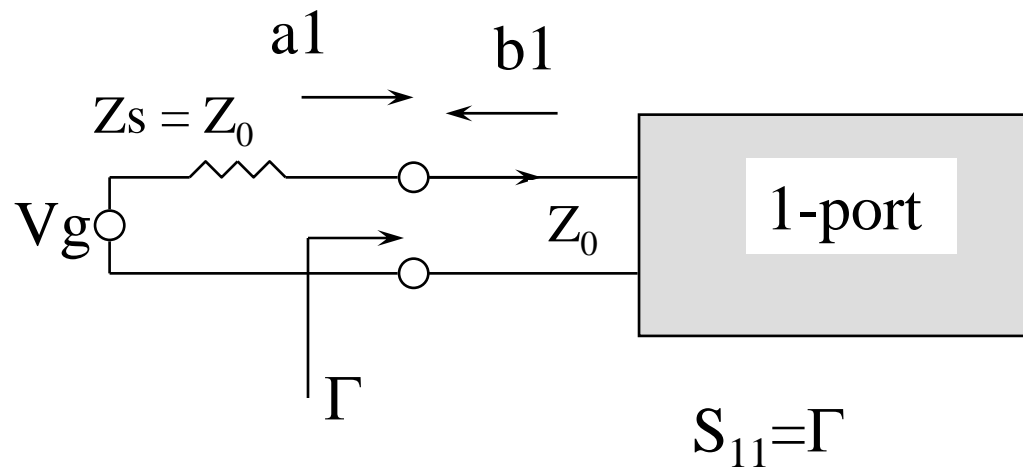Note...the input and output are terminated in Z_0



GRAPHICAL VIEW OF S-PARAMETERS

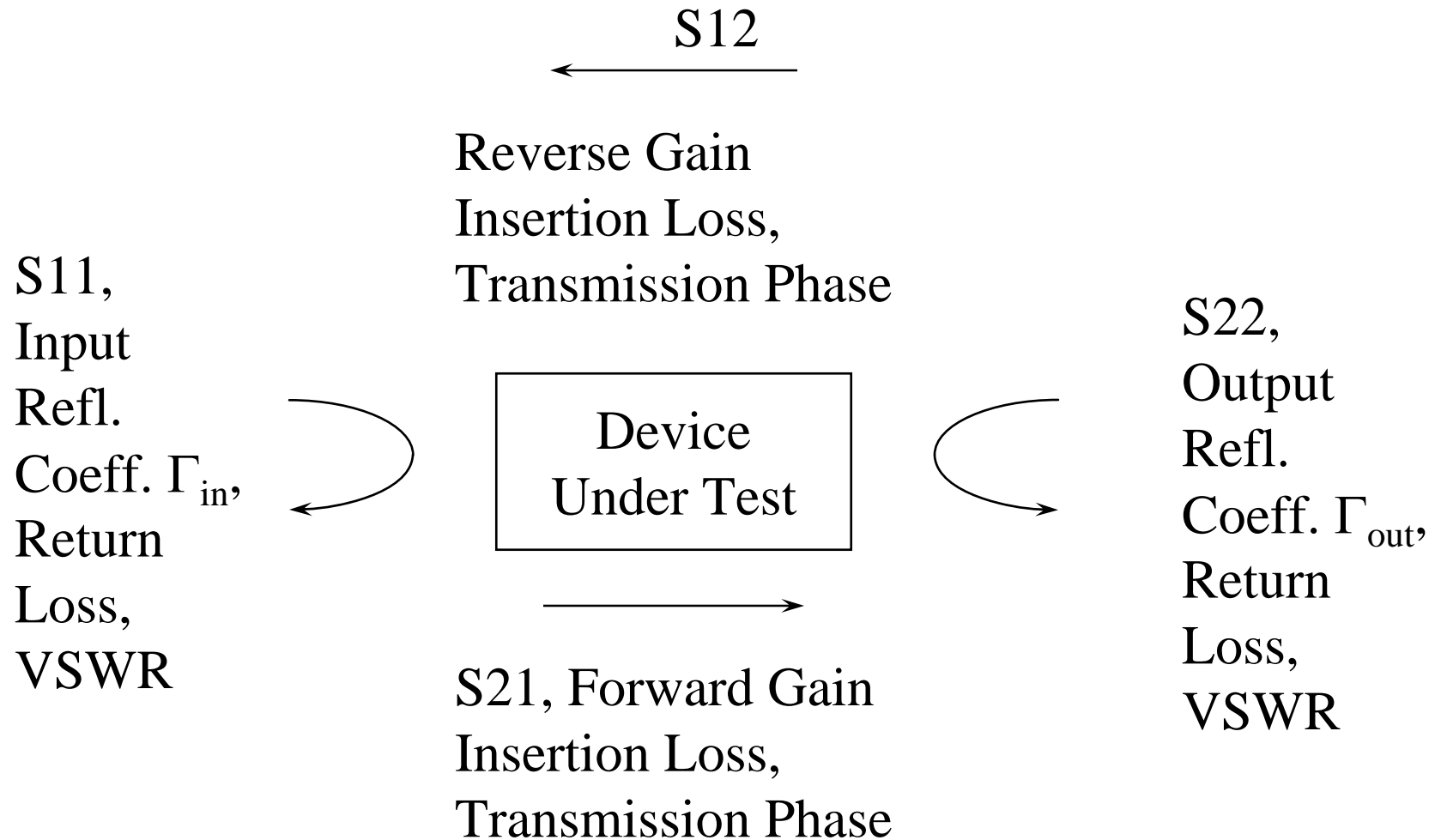


S-Parameters in Decibels

	dB	Meaning or interpretation
S_{11}	$20 \log_{10} S_{11} $	Corresponds to the algebraic negative of the input return loss of a 2-port with an R_0 termination on the opposite port.
S_{12}	$20 \log_{10} S_{12} $	Reverse isolation (active device or amplifier), or algebraic negative of the insertion loss (I.L.) for a passive device, with R_0 at ports 1 and 2.
S_{21}	$20 \log_{10} S_{21} $	Power gain (active device or amplifier), or algebraic negative of the insertion loss (I.L.) for a passive device, under matched R_0 at ports 1 and 2.
S_{22}	$20 \log_{10} S_{22} $	Corresponds to the algebraic negative of the output return loss of a 2-port with an R_0 termination on the opposite port.

WHAT TO EXPECT

Ideal Lossless T-line

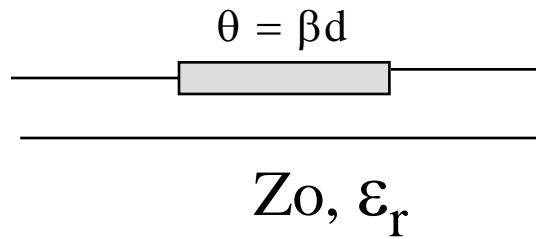



$$\begin{aligned} S_{11} &= S_{22} = 0 \\ S_{21} &= S_{12} = 1e^{-j\theta} \\ S_{21\text{DB}} &= 0 \end{aligned}$$

Ideal “X” dB Attenuator



$$\begin{aligned} S_{11} &= S_{22} = 0 \\ S_{21} &= S_{12} = x e^{-j\theta_{\text{pad}}} \\ S_{21\text{DB}} &= \mathbf{X} = 20 \log(|S_{21}|) \\ x &= 10^{-\mathbf{X}/20} \end{aligned}$$

Ideal “G” dB Gain Amp

 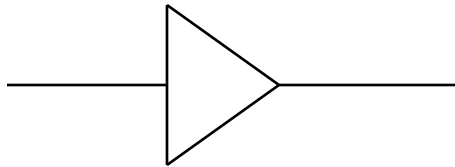


$$\begin{aligned} S_{11} &= S_{22} = 0 = S_{12} \\ S_{21} &= g_v e^{-j\theta_{\text{amp}}} \\ S_{21\text{DB}} &= \mathbf{G} = 20 \log(S_{21}) \end{aligned}$$


$$g_v = 10^{\frac{\mathbf{G}}{20}}$$

WHAT TO EXPECT: Ideal Filters


Ideal Band Pass

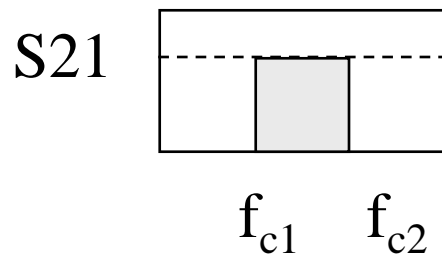

Ideal Low Pass

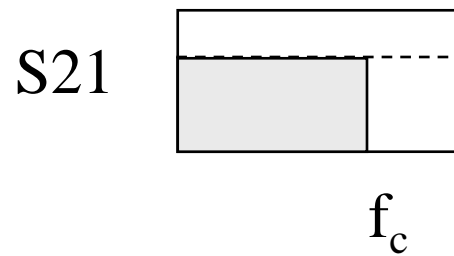

Ideal High Pass

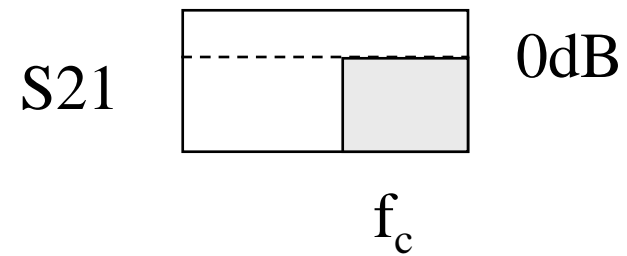

GENERAL “IN-BAND”

$$S_{11}=S_{22}=0$$

$$S_{21}=S_{12}=1e^{-j\theta(f)}$$

$$S_{21}(\text{dB})=S_{12}(\text{dB})=0\text{dB}$$

GENERAL “OUT-OF-BAND”

$$|S_{11}|=|S_{22}|=1$$

$$S_{21}=S_{12}=0$$

$$S_{11}(\text{dB})=S_{22}(\text{dB})=0\text{dB}$$