

# RC Integrator and Differentiator

## KEY PRINCIPLES TO BE DEMONSTRATED:

Applications of the charging and decay times of RC circuits

## EQUIPMENT (LOCATION):

Pasco function generator (Cabinet #1, Shelf #3)

$10\mu\text{F}$  capacitor (Cabinet #1, Shelf #3)

$20\text{k}\Omega$ ,  $1\text{M}\Omega$  resistors (Cabinet #1, Shelf #3)


Connection board[with attached variable capacitor] (Cabinet #1, Shelf #3)


Dual trace oscilloscope (Cabinet #1, Shelf #3)

## SET-UP/PROCEDURE:
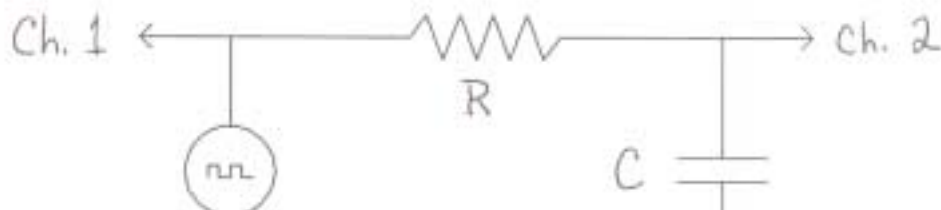
### Integrator

- Set up circuit as shown below with the oscilloscope on dual trace and auto trigger.




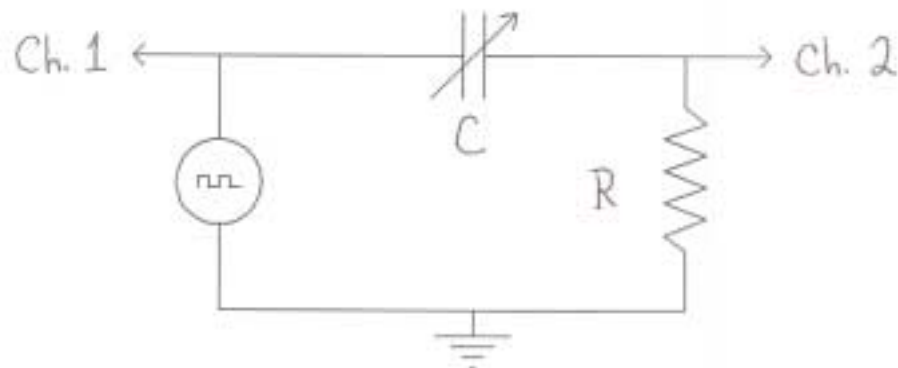

- With the tunable capacitor tuned to 295pF set the function generator to square wave at 60-100Hz and medium amplitude.
- To get a good picture on the scope set the time base to 2ms/div, Channel 1 to 5V/div and Channel 2 to 2V/div.
- Channel 2 should show spikes(delta functions) at the discontinuities of the square wave(series of step functions). Thus the circuit outputs the derivative of the input.
- The capacitor can be varied to show the change in slope of the output.
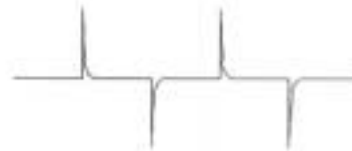
#### THINGS TO NOTE:

- The tunable capacitor varies between 50 and 295pF.
- Insure proper grounding of the oscilloscope probes to prevent rather large 60Hz waves from dominating the screen.



#### INTEGRATOR

$$T = 1/150\text{Hz} = 6.6\text{ms}$$

$$RC = 2 \times 10^4 (10 \times 10^{-6}) = 200\text{ms}$$

$$RC \gg T$$

#### DIFFERENTIATOR

$$T = 1/100\text{Hz} = 10\text{ms}$$

$$RC = 10^6 (295 \times 10^{-12}) = .3\text{ms}$$

$$RC \ll T$$